

Simulation Procedures for Hspice

How to Define FinFET Transistors

Fig 1. Shows an example of the typical structure of a FinFet. In this technology, the designer has freedom to control the sizes of transistors by means of the channel length (parameter l), the number of fins (parameter n_{fin}), and the number of fingers (parameter n_f).

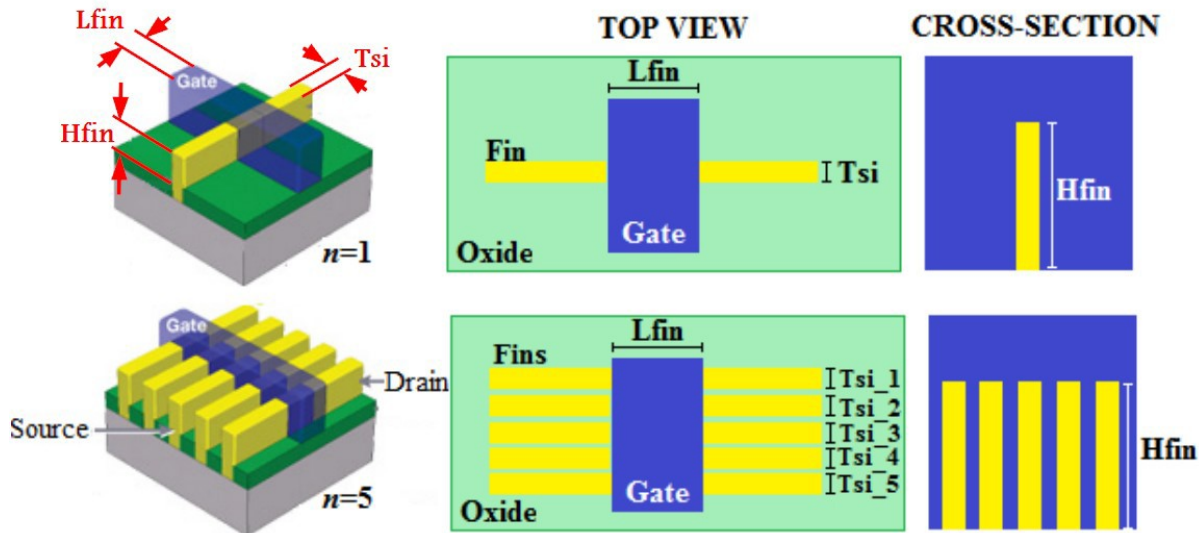


Figure 1. FinFet Structure, *source*: Zimpeck, et al. "FinFET cells with different transistor sizing techniques against PVT variations". ISCAS 2016.

An example Hspice netlist for the inverter in Fig.2 is shown:

```
M1 Q A Vdd Vdd pmos_lvt (nfin = 4 l = 16n nf=2 )
M2 Q A Vdd Vdd nmos_lvt (nfin = 4 l = 16n nf=2 )
```

 


Figure 2 Inverter Example

How to Run Hspice

- 1) Un-compress the models and save them in your <simulation folder>
- 2) In text editor, create a netlist and save it in the <simulator folder> with extension .sp or .cir (in this example Comparator.sp)

***** START EXAMPLE COMPARATOR NETLIST *****

```
.option post runlvl=6
.include '<PATH>/<TT MODELFILE>.inc'
.TEMP 80
m1 p clk 0 0 nmos_lvt (nfin = 4 l = 16n nf=2) m2a xn inp p 0 nmos_lvt(nfin = 4 l = 16n nf=2 ) m2b xp inn p 0
nmos_lvt(nfin = 4 l = 16n nf=2 )
```

```

m3a outn outp xn 0 nmos_lvt (nfin = 4 l = 16n nf=2 ) m3b outp
outn xp 0 nmos_lvt (nfin = 4 l = 16n nf=2 ) m4a outn outp 1 1
pmos_lvt (nfin = 4 l = 16n nf=2 ) m4b outp outn 1 1 pmos_lvt
(nfin = 4 l = 16n nf=2 ) m5a outn clk 1 1 pmos_lvt (nfin = 4 l =
16n nf=2 ) m5b outp clk 1 1 pmos_lvt (nfin = 4 l = 16n nf=2 )
m6a xn clk 1 1 pmos_lvt (nfin = 4 l = 16n nf=2 )
m6b xp clk 1 1 pmos_lvt (nfin = 4 l = 16n nf=2 ) C1 outp 0
25f
C2 outn 0 25f

```

```

vdd 1 0 dc 0.9
vinn inn 0 0.6
vinp inp 0 0.61

```

```

*****

```

```

Vclk clk 0 pulse (0 'pvdda' '0.4*per' '0.1*per' '0.1*per' '0.4*per' 'per')
.param freq=250Meg per='1/freq' pvdda=0.9
.tran 'per/50' '20*per'
.probe TRAN V(*)

```

```

.alter
.include '<PATH>/<FF MODELFILE>.inc'
.alter
.include '<PATH>/<SS MODELFILE>.inc'

```

```

.end
***** END COMPARATOR NETLIST *****

```

- 3) set any environment variables required to access your Hspice license and add Hspice executables folder to your path. (This part is dependent on your particular installation and environment.)
- 4) run the netlist by entering:

hspice Comparator.sp > Comparator.out

```

jsalinas@anubis.eecg[~/Desktop/ECE1352/2020/PTM-MG/tests]> hspice Comparator.sp > Comparator.out
>info:      ***** hspice job concluded
>info:      ***** hspice job concluded
>info:      ***** hspice job concluded

```

- 5) Notice how some files with the initials Comparator.* are created (Advice: study what each file is)

Comparator.ic0	Comparator.ic2	Comparator.sp	Comparator.tr0	Comparator.tr2
Comparator.ic1	Comparator.out	Comparator.st0	Comparator.tr1	

- 6) Open the waveform viewer (in this case spice explorer)


- a. sx <output file we want to plot>

```


jsalinas@anubis.eecg[~/Desktop/ECE1352/2020/PTM-MG/tests]> sx Comparator.tr0

```

7) plot your results

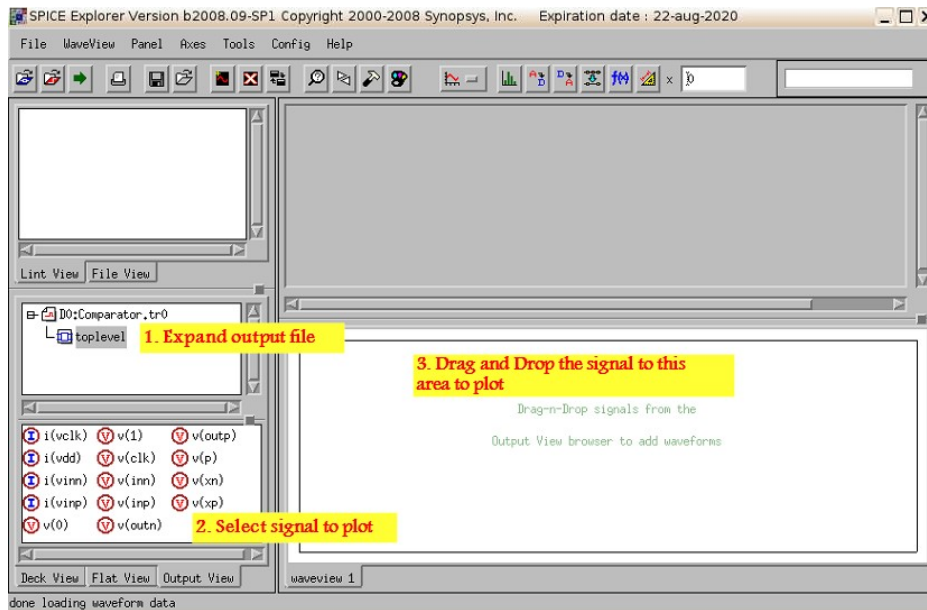

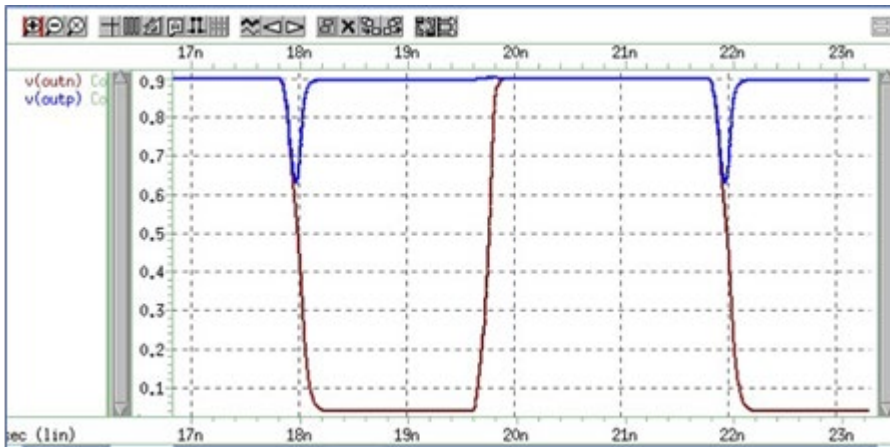For example, these are the outputs of the comparator:



- Or you can export the data and plot in other external tools

How To Setup Process Corner Simulation in Hspice

The model may include models for Typical, Slow PMOS/Slow NMOS (SS) and Fast PMOS/Fast NMOS (FF).

In Hspice, with the .include command, we can point to the model file for each corner. For example for TT corner, the command is:

```
.include './ece1352_models/hp_model_finfet16_TT.inc'
```

In the example netlist (Comparator.sp), the command “.alter” is used to modify the netlist to point to SS and FF corner models

```
.alter
```

After simulating this netlist, three output files are created, each output file corresponds to each process corner.

```
jsalinas@anubis.eecg[~/Desktop/ECE1352/2020/PTM-MG/tests]> sw Com
Comparator.ic0      Comparator.ic2      Comparator.sp      Comparator.tr0      Comparator.tr2
Comparator.ic1      Comparator.out      Comparator.st0     Comparator.tr1
```